

EMETTEUR CLAMP - BGV-2001

Lorsque j'ai construit mon premier émetteur AM, vers la fin des années 50, il m'était impossible, pour des raisons pécuniaires, de me procurer un transfo de modulation QRO.

Je m'étais donc tourné vers la modulation « Clamp », à porteuse contrôlée, se contentant d'une partie BF simplifiée. Mais, comme toute modulation grille, le rendement moyen de l'étage HF reste médiocre et nécessite, soit un gros tube (j'utilisais à l'époque une 8236), soit plusieurs tubes en parallèle.

C'est cette dernière solution, plus pratique, que je vous propose maintenant :

1) ETAGES HF

Le VFO (EF184) de type ECO, sur 1,75 MHz, donnera toute satisfaction si son circuit oscillant est de bonne qualité diélectrique (condos mica) et mécanique (CV, self et câblage rigides).

Il est suivi d'un étage DRIVER/DOUBLEUR, sur 3,5 MHz, qui attaque un PA composé de 3 x 6146B en parallèle.

Le circuit de sortie en π , est prévu pour une impédance de sortie standardisée de 50 Ω .

2) ETAGES BF

La modulation « Clamp », agit sur la tension d'écran du PA, qui varie selon l'intensité de la voix. On l'appelle aussi modulation « à taux constant ». Elle se contente de peu de composants (préampli micro par ECC81 et tube Clamp EL86 en pseudo-triode), mais exige une résistance de charge de forte puissance. Elle fait ainsi l'économie d'un transfo de modulation, toujours lourd, encombrant et onéreux. J'ai aussi prévu une petite contre-réaction, améliorant la qualité de la modulation.

3) ALIMENTATION

Elle n'utilise qu'un seul transformateur, suivi d'un redressement en pont, délivrant les deux hautes-tensions nécessaires, ainsi que le chauffage filaments.

ATTENTION à la HT ! Demeurez extrêmement PRUDENTS.

J'ai moi-même réalisé et mis au point cet ensemble qui peut délivrer plus de 50 WHF, en pointe de modulation.

Les tubes utilisés sont de la série NOVAL, mais il est permis de les remplacer par ceux de la série OCTAL, à la robustesse légendaire et encore disponible :

- EF184 = 6AC7
- EL83 = 6AG7
- ECC81 = 6SN7 (découpler cathode 1^{ère} triode)
- EL86 = 6Y6 (à défaut 6V6 ou 6L6)

Je reste à votre disposition, en cas de besoin.

Amitiés à tous


Jean-Pierre (F6BGV)

四百九

18

3 x 6 1/4 B

10

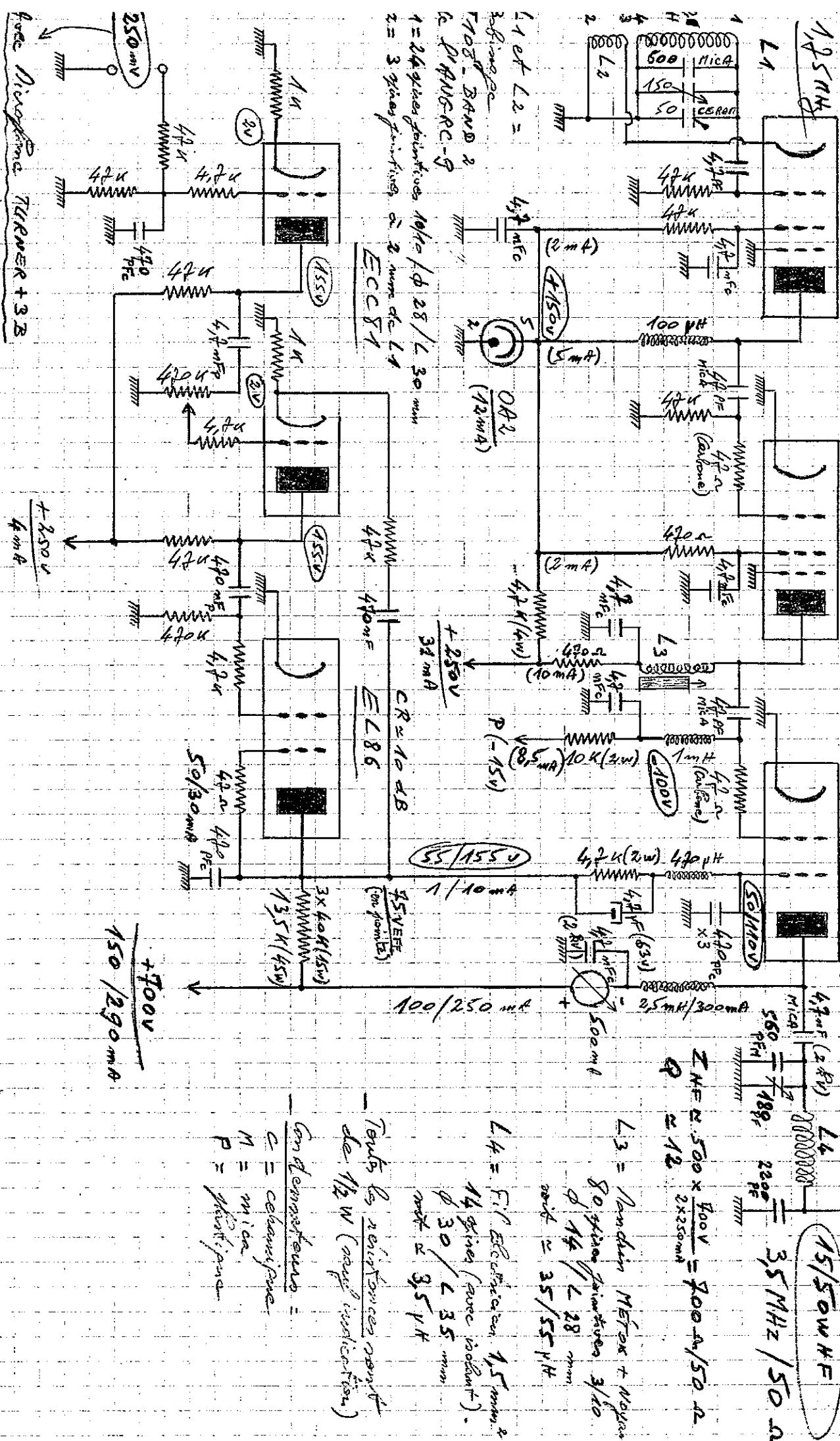

Action 3 (50 mV) → PSE ASsez
 Action 35 (150 mV) → TRES BIEN
 Action 4 (250 mV) → MAXIMUM (TRES EFFICACE)
 Action 5 (500 mV) → Eutanase

ENTREUR "CLAMP"

com - Niene. VENEMBRE

L-C LINK DESIGN

trinsic information as those currently in the Handbook,¹ but give it in terms of inductance and capacitance, rather than reactance. The values shown apply at a frequency of 3.5 Mc. and must be modified appropriately for other frequencies. Average values for the various amateur bands can be found as follows:

3.5 Mc. — Use as given.

7 Mc. — Divide L and C values by 2.

14 Mc. — " " " " " 4.

21 Mc. — " " " " " 6.

28 Mc. — " " " " " 8.

An approximate value for the plate load resistance can be found from

$$500 \times \frac{\text{Plate Voltage}}{\text{Plate Current in ma.}}$$

¹ From the article by R. C. Meidke, WPRSL, in November 1955 QST.

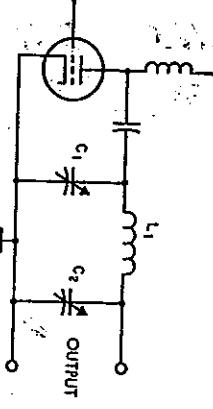


Fig. 1—Pi-network tank circuit, with component designations used in the chart. The plate load resistance is the resistance looking into the left-hand side of the network when an actual load is connected to the "output" terminals.

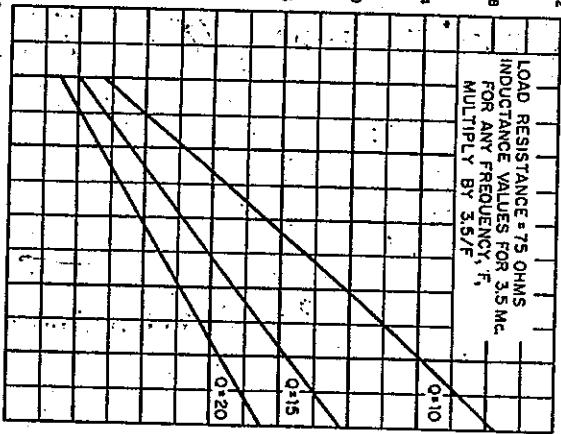


Fig. 2—Tank capacitance as a function of plate load resistance. The tank capacitance is dependent only on the tank C_1 , so this chart applies regardless of the value of the actual load resistance.

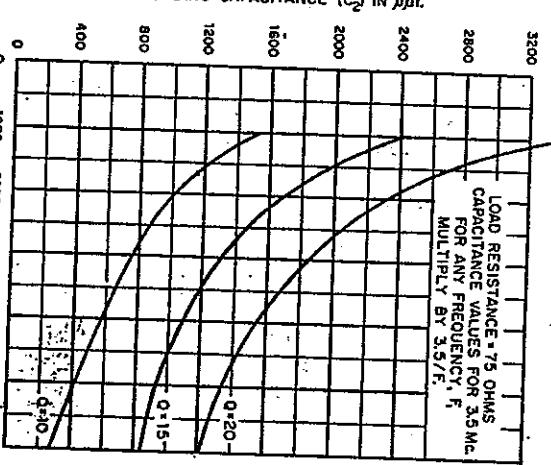


Fig. 3—Capacitance values for 3.5 Mc., multiplied by 3.5/F, for any frequency F , multiplied by 3.5/F.

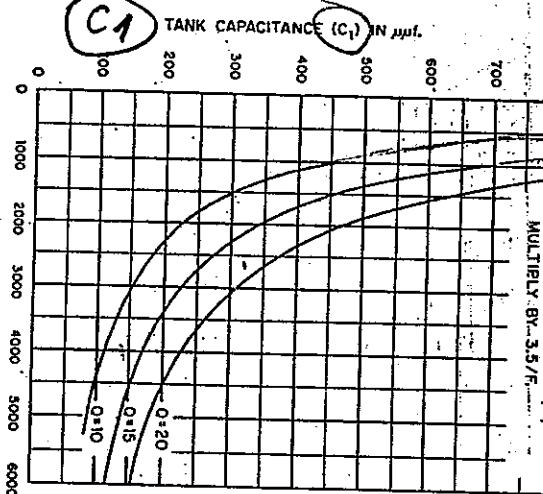


Fig. 4—Output or loading capacitance as a function of plate load resistance, for an actual load of 75 ohms.

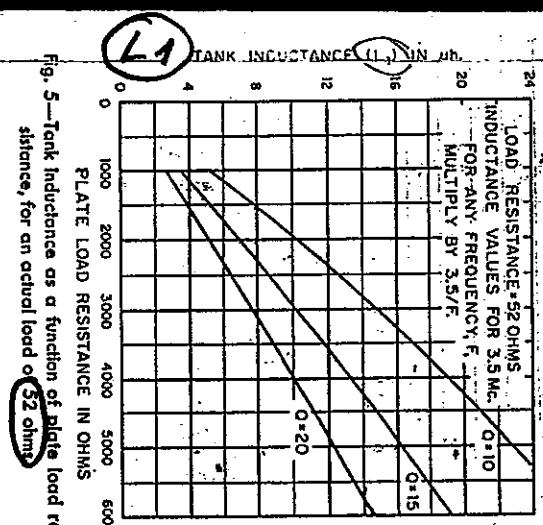


Fig. 5—Tank inductance as a function of plate load resistance, for an actual load of 75 ohms.

fully wide range. When using a fixed tank inductance calculated as described above it is advisable to select a Q of at least 15, since the operating Q will decrease with increasing frequency in the band.

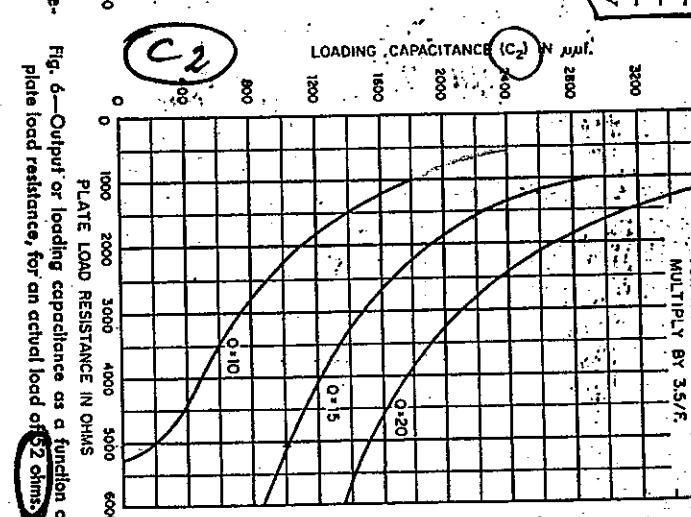


Fig. 6—Output or loading capacitance as a function of plate load resistance, for an actual load of 75 ohms.

The function of the A.R.R.L. QSL Bureau system is to facilitate delivery to amateurs in the United States, its possessions, and Canada of those QSL cards which arrive from amateur stations in other parts of the world. Its operation is made possible by volunteer managers in each W, K and VE call area. All you have to do is send your QSL manager (see list below) a stamped self-addressed envelope about 4½ by 9½ inches in size, with your name and address in the usual place on the front of the envelope and your call printed in capital letters in the upper left-hand corner.

W1, K1 — G. L. DeGraffenreid, WIGKX, 109 Gallup St., North Adams, Mass.
W2, K2 — Robert Stark, W6LG, P.O. Box 261, Grapetown, Tex.
W3, K3 — Jessie Bieberman, W3KT, P.O. Box 400, Baldwin, Pa.
W4, K4 — Thomas M. Moss, W4HYW, Box 644, Municipal Airport Branch, Atlanta, Ga.
W5, K5 — Robert Stark, W6LG, P.O. Box 261, Grapetown, Tex.
W6, K6 — Horace R. Greer, W6TJ, 414 Fairmount Avenue, Oakland, Calif.
W7, K7 — Sulam, W4HWW, Box 644, Municipal Airport Branch, Atlanta, Ga.
W8, K8 — Walter E. Musgrave, W8NGW, 1245 E. 187th St., Cleveland 10, Ohio.
W9, K9 — J. F. Oberg, W9DSO, 2801 Gordon Drive, Elmhurst, Ill.
W10, K10 — Alva A. Smith, W10DMA, 228 East Main St., Caldonia, Minn.
W11 — L. F. Rader, VE1FFQ, 125 Henry St., Halifax, N. S.
W12 — George C. Goode, VE1YYA, 188 Lakeview Ave.,

A.R.R.L. QSL BUREAU

Pointe Claire, Montreal 33, Que.
VE3 — Leslie A. Whitteman, VE3QE, 32 Sylvia Crescent, Hamilton, Ont.

VE4 — Len Cuff, VE4LC, 288 Rutland St., St. James, Man.

VE5 — Fred Ward VE5OP, 899 Connaught Ave., Moose Jaw, Sask.

VE6 — W. R. Savage, VE6EO, 833 10th St., North Lethbridge, Alta.

VE7 — H. R. Hough, VE7HR, 1684 Freeman Rd., Victoria, B. C.

VE8 — W. L. Geary, VE8AW, Box 534, Whitehorse, Y.T.

VO1 — Ernest A. Volak, P.O. Box 8, St. John's, Newfoundland.

VO2 — Douglas B. Rithey, Dept. of Transport, Goose Bay, Labrador.

KP4 — E. W. Mayer, KP4KD, Box 1061, San Juan, P. R.

KH6 — Andy H. Fuchikami, KH6BA, 2543 Nauuan Dr., Honolulu, T. H.

KJ7 — KJ7CP, 310-10th Ave., Anchorage, Alaska.

KZ5 — Catherine Howe, KZ5KA, Box 407, Balboa, C. Z.


IS YOURS ON FILE
WITH YOUR QSL MGR?

NAME _____
YOUR OWN NAME

YOUR HOME TOWN

U.S.A. _____
91%

CALCULS DU CIRCUIT EN π (F6BGV)

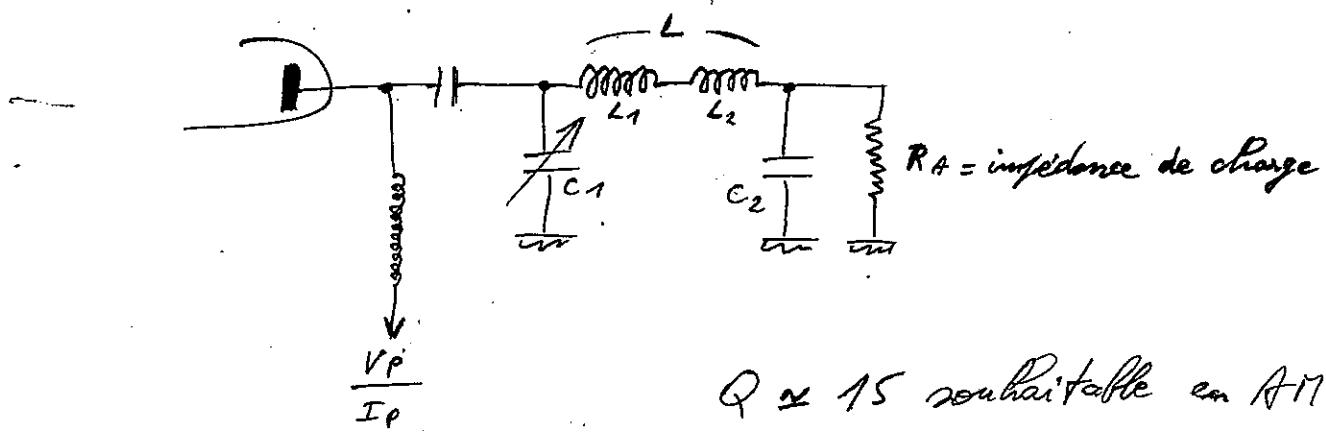

$Q \approx 15$ souhaitable en AM
(10 en CW)

$$R_P = \frac{V_p}{2 \times I_p}$$

$$X_{C_1} = \frac{R_p}{Q}$$

$$X_{L_1} = \frac{R_p}{Q}$$


$$X_{C_2} = R_A \sqrt{\frac{R_p}{R_A(Q^2 + 1) - R_p}}$$

$$X_{L_2} = \frac{R_A^2 \cdot X_{C_2}}{R_A^2 + X_{C_2}^2}$$

$$X_L = X_{L_1} + X_{L_2}$$

$$C_{PF} = \frac{1.000.000}{6,28 \times F_x \text{ MHz} \times X_C}$$
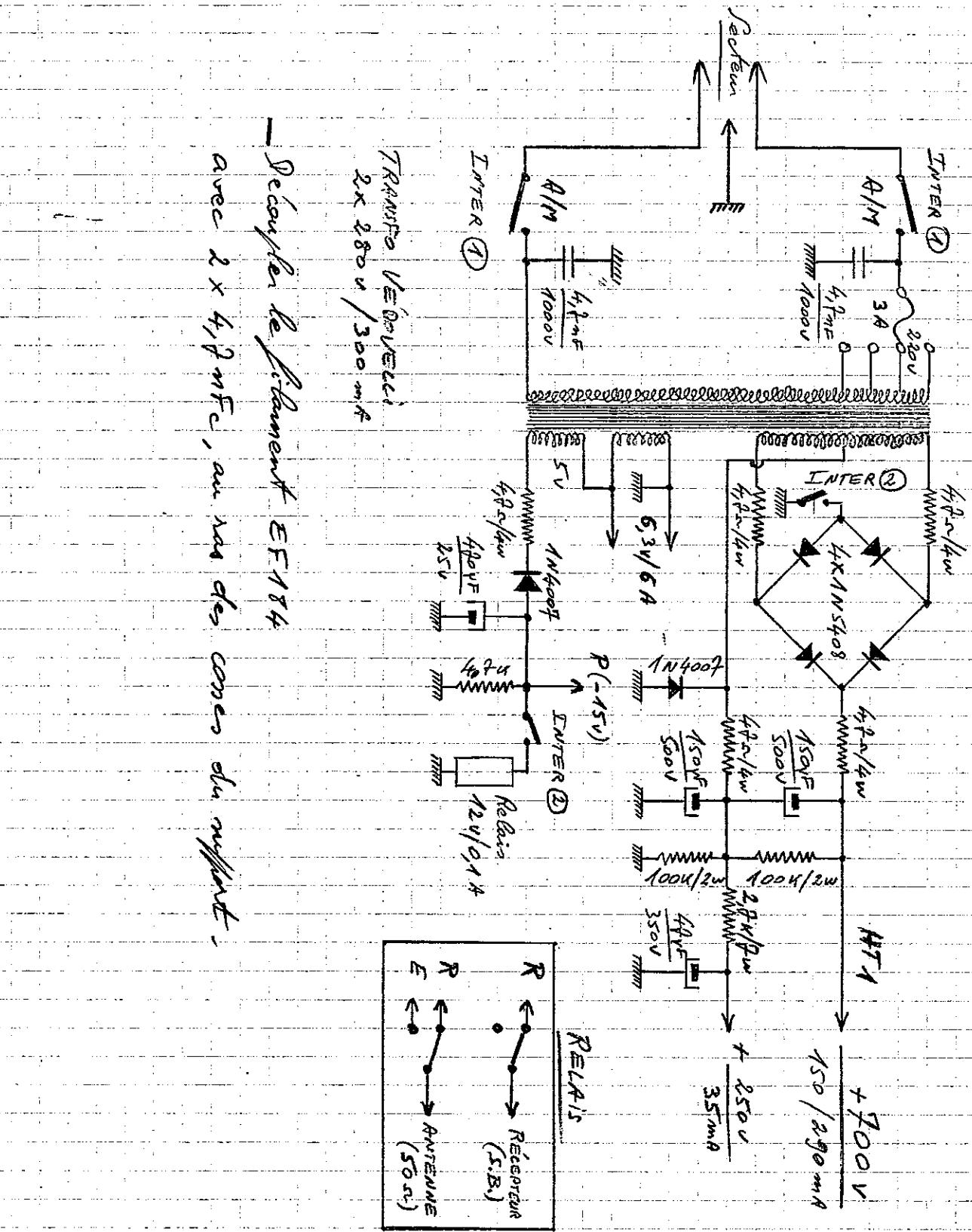
$$\frac{L}{\mu H} = \frac{X_L}{6,28 \times F_{MHz}}$$



Attention = Name Inter (2)
current, 200 or 350 v max

~~Le couper le lâchement EFT~~

TRANS DEVEL
2x 280n / 300m

INTERVIEW

三

THE BAPTIST

100% +

1000/051

卷之三

Jean-Pierre VÉMÈBRE

2001
FEB 9