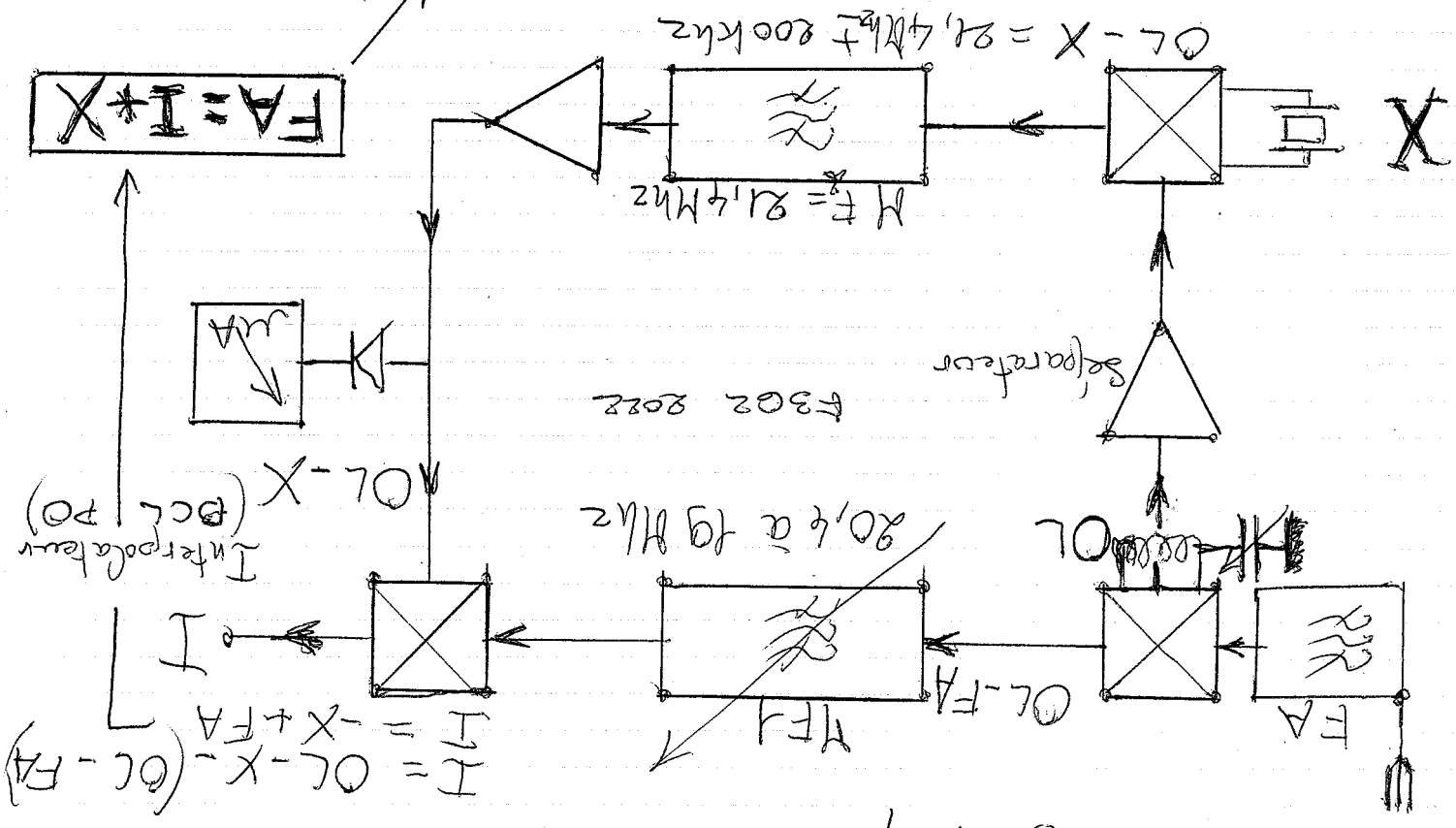


CONVERTISSEUR OC STABILISÉ

Synoptique



EXEMPLES de GAINES REÇUES

F @ QUANTZ (X) F REÇUE (FA) OSCILLATEUR LIBRE (OL)

3	3,55 / 4,65	24,400
4	4,55 / 5,65	25,400
5	5,55 / 6,65	26,400
6	6,55 / 7,65	27,400
9	9,55 / 10,65	30,400
13	13,55 / 14,65	34,400
17	17,55 / 18,65	38,400
20	20,55 / 21,65	41,400
27	27,55 / 28,65	48,400
28	28,55 / 29,65	49,400
MF1 = 20,850 / 19,900		
Interpolateur 0,550 - 1650 = I		

